

AI Summary

Here's a concise, exam-oriented summary of the study notes:

* **Experiment Objective:** To study the design and operation of inverting and non-inverting amplifier circuits using an op-amp.

* **Key Circuit Types & Gain Formulas:**

*

* **Procedure:**

1. C

* **Observations:** Record input frequency, input voltage (V_i p-p), output voltage (V_o p-p), and the calculated gain for both amplifier configurations.

* **Result:** Successfully designed, set up, and obtained output waveforms for both inverting and non-inverting op-amp amplifiers, with their experimental gains determined.